

2023 MOCK APPLIED ELECTRICITY 1
OBJECTIVE- FEBRUARY, 2023.

SUBJECT: APPLIED ELECTRICITY.

DURATION: 2 HOURS

[100 MARKS]

Answer all the questions.


Circle the correct option

1. A solid-state device that has three pn junction is
A. triac B. field effect transistor
C. bipolar transistor. D. light emitting diode
2. A Zener diode is used as
A. current reference diode
B. voltage reference diode
C. high power diode
D. high frequency diode
3. A junction field effect transistor
A. is a voltage-controlled device
B. is a current – controlled device
C. has a low input impedance
D. has a high voltage gain
4. A component that is used to smooth d.c. output in rectifier circuit is
A. capacitor B. resistor
C. diode D. inductor
5. The function of a stabilizer circuit in a power supply unit is to
A. step-up a.c. voltage B. step-down d.c. voltage
C. reduce ripples D. provide a steady output
6. Triacs are used as
A. capacitor discharging device
B. full-wave power-controlled device
C. half-wave power-controlled device
D. voltage doubler device
7. Thyristors are mainly used for
A. amplification B. inverting circuit
C. limiting circuit D. speed control
8. The binary number 10001_2 , converted into its decimal equivalent is
A. 25 B. 15 C. 17 D. 5
9. A silicon-controlled rectifier is a
A. three-layer, three terminal device
B. two-layer, two terminal device
C. three-layer, four terminal device
D. four-layer, three terminal device
10. The binary equivalent of the hexadecimal number 2AC is
A. 0101 0101 1000
B. 0101 0101 0001
C. 0010 0011 1000
D. 0010 1010 1100
11. The sum of the binary numbers 10001_2 and 111_2 is
A. 10010 B. 10011
C. 11000 D. 11001
12. In a stabilized power supply block diagram, the rectifier block comes after the
A. transformer B. voltage regulator
C. d. c output D. rectifier block
13. The function of a voltage stabilizing circuit is to
A. double the load resistor
B. compensate for the voltage drop in the rectifying diode
C. keep the load current constant
D. keep the power dissipated in the load high
14. The total resistance of R_1 and R_2 resistors in parallel
A. $R_1 + R_2$ B. $\frac{1}{R_1} - \frac{1}{R_2}$
C. $\frac{R_1+R_2}{R_1R_2}$ D. $\frac{R_1R_2}{R_1R_2}$
15. A device that changes an a.c. input voltage into d.c. voltage is called
A. a rectifier B. a stabilizer
C. a transformer D. an inverter
16. A logic gate is an electronic circuit which
A. does not work on binary numbers
B. makes a logic decision
C. does not alternate between 0 and 1
D. allows electronic flow in one direction
17. The value of a resistor with brown and orange colour bands is
A. $1000K\Omega$ B. $100K\Omega$
C. $10K\Omega$ D. $1K\Omega$

37. The random motion of holes and free electrons due to thermal agitation is called
 A. diffusion B. ionization
 C. crystallization D. none of the above
38. Which stage of a d.c. power supply uses a Zener diode as the main component?
 A. rectifier B. regulator
 C. filter D. transformer
39. The number of p-n junction within a bipolar transistor is
 A. 1 B. 2 C. 3 D.
40. The nominal value of a resistor with brown, black, orange, and silver band is
 A. $1000\text{K}\Omega \pm 10\%$ B. $100\text{K}\Omega \pm 10\%$
 C. $10\text{K}\Omega \pm 10\%$ D. $1\text{K}\Omega \pm 10\%$

Use the figure below to answer questions


41 – 44

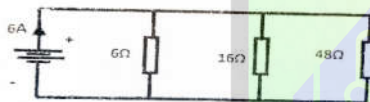

41. The total resistance of the circuit is
 A. 0.25Ω B. 4.00Ω
 C. 18.00Ω D. 70.00Ω
42. The current flowing through the 16Ω resistor is
 A. 0.34A B. 1.35A C. 1.50A D. 6.00A
43. The power dissipated in the 6Ω resistor is
 A. 144W B. 96W C. 36W D. 12W
44. The supply voltage to the circuit above is
 A. 12V B. 24V
 C. 36V D. 2.4V

Use the figure below to answer questions


45 – 46

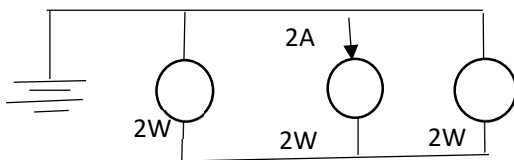

45. The total power dissipated in the circuit is
 A. 0.67W B. 2.00W
 C. 6.00W D. 8.00W
46. The voltage drop across the parallel circuit is
 A. 1V B. 3V
 C. 4V D. 6V
47. The voltage across an appliance of Q coulombs of charge C , while dissipating W joules of energy is
 A. $\frac{W}{Q}$ B. $\frac{W}{Q^2}$
 C. $\frac{W^2}{Q}$ D. $\frac{Q}{W}$
48. The unit of the frequency of an alternating current signal is
 A. Weber B. Coulomb C.
 Hertz D. Farad
49. The rotating part of a d.c motor is the
 A. Yoke B. Brush
 C. Field D. Armature
50. The purpose of a filter in a power supply system is to
 A. obtain unidirectional but unstable output
 B. increase ripples in output voltage and current
 C. smoothen out ripples in output voltage and current
 D. provide pulsating output
51. The waveforms displayed on the screen of an oscilloscope can be made sharp by adjusting the
 A. intensity control
 B. focus control
 C. vertical gain control
 D. sweep selector control
52. Voltage that causes currents in the rotor assembly of a split-phase motor are produced by electromagnetic
 A. repulsion B. attraction
 C. induction D. force


Use the figure below to answer questions

48 – 50

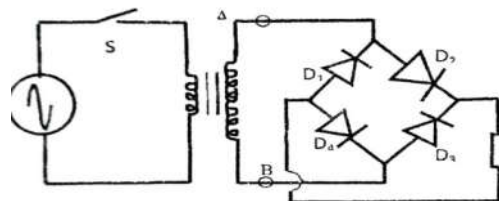

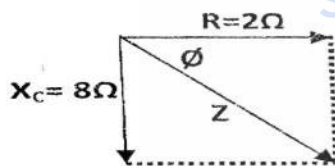53. The name of the circuit is
 A. diode circuit
 B. centre-tapped rectifier circuit
 C. bridge rectifier circuit
 D. half-wave rectifier circuit
54. Which of the diodes will conduct when the voltage at **A** is positive with respect to **B**?
 A. D_1 and D_3 B. D_2 and D_4
 C. D_1 and D_2 D. D_1 and D_4
55. Which of the diodes will conduct when the voltage at **B** is positive with respect to **A**?
 A. D_1 and D_3 B. D_2 and D_4
 C. D_1 and D_2 D. D_1 and D_4
56. A material on which a transistor is mounted to prevent overheating is called
 A. dissipater B. shield
 C. heat sink D. thermal runaway
57. In an A.C circuit, the ratio of the power in kilowatts to the kilovolt ampere is the
 A. power factor B. efficiency
 C. reactive power D. form factor
58. Conductors carrying current meet at a point and the total current at that point is zero. This is
 A. lenz's law B. ohm's law
 C. Kirchhoff's law D. faradays law

The figure below is a phasor diagram of an RC circuit. Use it to answer questions 58 and 59




59. The angle ϕ is
 A. -75.90° B. -16.56°
 C. -14.04° D. -8.25°
60. The total impedance z is
 A. 68.00Ω B. 16.00Ω
 C. 10.00Ω D. 8.25Ω
61. The principle of electromagnetic induction is used in the operation of
 A. potentiometer B. rheostat
 C. alternator D. electric iron
62. Earthing is employed in installation work in order to

- A. prevent electric shock
 B. prevent leakage current
 C. insulate the electrical appliances
 D. keep the current constant

63. The electrostatic distribution in a thermionic triode is done by
 A. cathode B. glass envelop
 C. anode D. grid
64. An electrical machine that has its field windings connected to the armature is said to be
 A. separately-excited B. self-excited
 C. synchronous D. polyphase
65. Convert 2_{10} to a binary number.
 A. 01_2 B. 100_2 C. 11_2 D. 10_2
66. What is the sum of the binary numbers 1001111 and 11111 ?
 A. 1100111_2 B. 1101110_2
 C. 1011111_2 D. 1001111_2
67. Which of the following is not true of a series RLC circuit at resonance?
 A. $X_L = X_C$ B. $\omega = \sqrt{LC}$
 C. $Z = R$ D. $\omega = 1/\sqrt{LC}$
68. The current at which a fuse melts is known as
 A. current rating B. fusing factor
 C. rating factor D. fusing current
69. In a series generator, the only current flowing in the field equals
 A. armature current
 B. half the armature current
 C. twice the armature current
 D. 0.7071 of armature current

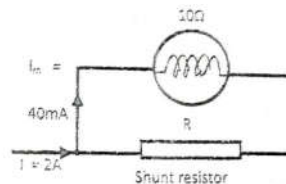
70. Which of the following sets of switches are used to control a point of light from two remotes positions
 A. Two, 2-way and one 2-way switches
 B. Two, 1-way and one intermediate switches
 C. Two, 2-way and one intermediate switches
 D. Two-2-way switches only

The figure below is a moving -coil instrument, use it to answer question 70 to 72



71. The value of current flowing through the shunt resistor, R is
 A. 2.040A B. 2.00A
 C. 1.960A D. 0.004A
72. Calculate the voltage across the circuit
 A. 0.04 V B. 0.40 V
 C. 10.00 V D. 20.00 V
73. What is the value of the shunt resistor R?
 A. 0.02 Ω B. 0.20 Ω
 C. 1.02 Ω D. 10.20 Ω
74. Which if the following converts electrical energy to mechanical energy?
 A. Generator B. transformer
 C. motor D. microphone
75. Which of the following converts sound energy to electrical energy?
 A. Generator B. transformer
 C. motor D. microphone
76. The maximum value attained by a waveform over half a cycle is known as its
 A. r. m. s value B. peak value
 C. average value D. form factor
77. In transistor amplifier circuits, the inter-stage capacitors are called
 A. series capacitor B. coupling capacitors
 C. decoupling capacitor D. mica capacitor
78. An auto transformer has
 A. one coil B. two coil
 C. three coil D. four coils
79. The phase difference between the starting and running windings in a single-phase induction motor is
 A. 90⁰ B. 120⁰
 B. 150⁰ D. 240⁰
80. Which of the following the starting and running windings in a single-phase induction motor is
 A. trunking B. plug
 C. conduit D. duct
81. A coil having an inductance of 0.4H is connected across a 230V,50Hz supply. The reactance of the coil is
 A. 314.3 Ω B. 125.6 Ω
 C. 62.8 Ω D. 2.5 Ω .
- Note : reactance, $X_L = 2\pi fL$
82. The type of electrical machine used for bulk electricity generation is the
 A. Single-phase a. c. generator
 B. Single phase a.c. motor
 C. Three Phase a.c. generator
 D. d. c generator
83. Permanent magnets are used in
 A. loud speakers B. relays
 C. electric bells D. electric fans
84. The power station which uses water as a motive force is?
 A. Hydro-power station
 B. Coal-fired power station
 C. Gas-fired power station
 D. Oil-fired power station
85. The electrical quantity that opposes the flow of electricity is
 A. Resistance B. Inductance
 C. Capacitance D. Reluctance
86. The purpose of the carbon brushes in a d.c. generator is to
 A. draw current from the armature coil
 B. minimize the effect of eddy currents
 C. increase the efficiency of the magnet
 D. draw current from the commutator
87. The device which ensures that the reading of a measuring instrument is always the same for a given measured quantity?
 A. operating devices
 B. deflecting devices
 C. controlling devices
 D. damping devices
88. The device which allows a small signal to control a large signal is known as
 A. diode B. capacitor
 C. transistor D. resistor
89. The generated voltage in a motor is called the
 A. supply voltage B. terminal voltage
 C. back emf D. source voltage
90. A socket outlet connected separately from the ring circuit is a
 A. Special breaker B. final sub-circuit
 C. main circuit D. spur
91. The power dissipated in a 9 Ω resistor when a current of 5A flows through it is
 A. 14W B. 45W
 C. 225W D. 405W

92. The features of an alternator are
- | | |
|--------------|----------------|
| I. Armature | II. Commutator |
| III. Exciter | IV. Slip ring |
- A. I and II only B. I and III only
 C. II and III only D. I, III and IV only.
- The figure is a configuration of capacitor in a circuit. use it to answer questions 93 to 95*

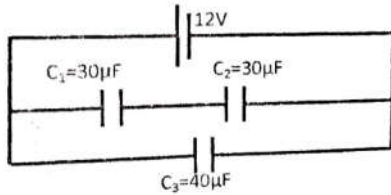

93. The equivalent capacitance of the two capacitors in series in the figure is
- | | |
|---------|----------|
| A. 15µF | B. 30µF |
| C. 60µF | D. 100µF |
94. What is the charge on the 40µF capacitor in the circuit?
- | | |
|-----------------------------------|-----------------------------------|
| A. $3.0 \times 10^5 \text{ C}$ | B. $4.8 \times 10^2 \text{ C}$ |
| C. $4.8 \times 10^{-4} \text{ C}$ | D. $3.3 \times 10^{-6} \text{ C}$ |

95. The voltage across C_2 is
- | | |
|--------|--------|
| A. 24V | B. 12V |
| C. 9V | D. 6V |
96. In the iron-moving instrument, damping is by means of
- | | |
|-----------------|----------------|
| A. Eddy-current | B. oil film |
| C. air-dashpot | D. hair-spring |
97. The angular frequency of a signal that has a frequency of 50Hz is
- | | |
|---------------|---------------|
| A. 50.0rad/s | B. 100.0rad/s |
| C. 314.2rad/s | D. 628.4rad/s |
- Note: $\omega = 2\pi f \text{ rad/s}$
98. A metal which is most commonly used as circuit conductor is
- | | |
|---------|-----------|
| A. Iron | B. Silver |
| C. Zink | D. Copper |
99. The ability of a material to allow magnetic field to pass through it is known as
- | | |
|-----------------|-----------------|
| A. Permeability | B. Conductivity |
| C. Permittivity | D. Retentivity |
100. The starter in a fluorescent lamp act as a/an
- | | |
|-------------|-------------|
| A. Resistor | B. fuse |
| C. switch | D. inductor |

END OF THE PAPER

ZeilaTech

Smart Learning Tools